

Circuit Note CN-0321

Circuits	
from the Lab	•
Reference Circuits	

Circuits from the Lab™ reference circuits are engineered and tested for quick and easy system integration to help solve today's analog, mixed-signal, and RF design challenges. For more information and/or support, visit www.analog.com/CN0321.

Devices Connected/Referenced			
AD5422	16-Bit Current and Voltage Output DAC		
AD5700-1	Low Power HART Modem with Internal RC Oscillator		
ADP2441	36 V, 1 A, Synchronous, Step-Down DC-to-DC Regulator		
ADuM3471	Quad Isolator with Integrated Transformer Driver and PWM Controller		
ADuM3482	Small, 3.75 kV rms Quad Digital Isolator		

Fully Isolated, Single Channel Voltage and 4 mA to 20 mA Output with HART **Connectivity**

EVALUATION AND DESIGN SUPPORT

Circuit Evaluation Boards

CN0321 Evaluation Board (EVAL-CN0321-SDPZ) System Demonstration Platform (EVAL-SDP-CB1Z)

Design and Integration Files

Schematics, Layout Files, Bill of Materials

CIRCUIT FUNCTION AND BENEFITS

This circuit provides a complete, fully isolated, analog output channel suitable for programmable logic controllers (PLCs) and distributed control system (DCS) modules that require standard 4 m A to 20 m A HART®1-compatible current outputs and unipolar or bipolar output voltage ranges. It provides a flexible building block for channel-to-channel isolated PLC/DCS output modules or any other industrial application that requires a fully isolated analog output. The circuit also includes external protection on the analog output terminals.

The AD5422 16-bit digital-to-analog converter (DAC) is software configurable and provides all the necessary current and voltage outputs.

The AD5700-1, the industry's lowest power and smallest footprint HART-compliant IC modem, is used in conjunction with the AD5422 to form a complete HART-compatible 4 mA to 20 mA solution. The AD5700-1 includes a precision internal oscillator that provides additional space savings, especially in channel-to-channel isolated applications.

PLC/DCS solutions must be isolated from the local system controller to protect against ground loops and to ensure robustness against external events. Traditional solutions use discrete ICs for both power and digital isolation. When multichannel isolation is needed, the cost and space of providing discrete power solutions becomes a big disadvantage. Solutions based on optoisolators typically have reasonable output regulation but require additional external components, thereby increasing board area. Power modules are often bulky and can provide poor output regulation. The circuit in Figure 1 uses the ADuM347x family of isolators and power regulation circuitry along with associated feedback isolation. External transformers are used to transfer power across the isolation barrier.

The ADuM3482 provides the UART signal isolation for the AD5700-1.

The ADP2441, 36 V step-down dc-to-dc regulator, accepts an industrial standard 24 V supply, with wide tolerance on the input voltage. It steps this down to 5 V to power all controller side circuitry. The circuit also includes standard external protection on the 24 V supply terminals, as well as protection against dc overvoltage of +36 V down to -28 V.

Grouits from the Lab™ circuits from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a laben vironmentat room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no events hall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any Circuits from the Lab circuits. (Continued on last page)

Fax: 781.461.3113 ©2013 Analog Devices, Inc. All rights reserved.

¹ HART is a registered trademark of the HART Communication Foundation.

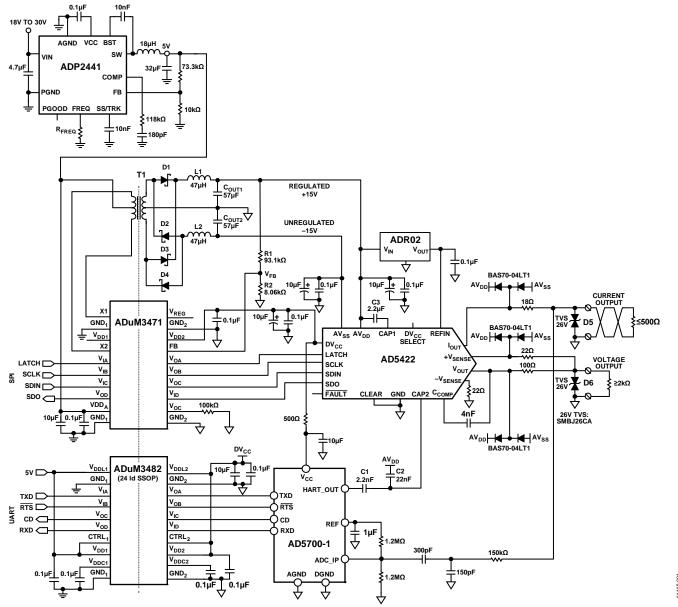


Figure 1. Functional Block Diagram (Simplified Schematic: All Connections and Decoupling Not Shown)

CIRCUIT DESCRIPTION

Analog Output

For industrial control modules, standard analog output voltage and current ranges include ± 5 V, ± 10 V, 0 V to +5 V, 0 V to +10 V, +4 mA to +20 mA, and 0 mA to +20 mA. The AD 5422 is a precision, fully integrated 16-bit DAC that offers a programmable current source and programmable voltage output designed to meet the requirements of industrial process control applications.

The AD5422 provides all the output ranges previously listed, with the current output ranges and voltage output ranges available on separate pins. An overrange feature of 10% is available on all the voltage ranges, and a 0 mA to 20 mA overrange is available on the current output. Analog outputs are short- and open-circuit protected.

The AD5422 has an on-board 10 ppm/°C reference. For higher performance over temperature, this design uses an ADR02 reference. The ADR02 is a 5 V precision reference that allows for an input voltage of up to 36 V. It has a 0.05% maximum accuracy error and a 3 ppm/°C maximum temperature drift. This drift contributes approximately 0.02% error across the industrial temperature range.

The AD5422 allows for an internal or external precision, current setting resistor for the current output circuitry. This design uses the internal current sensing resistor option; however, even higher accuracy can be achieved by using a precision external 15 k Ω resistor.

Circuit Note CN-0321

By leaving the DV $_{\rm CC}$ SELECT pin of the AD5422 floating, an internal 4.5 V power supply is connected to the DV $_{\rm CC}$ pin which is used as a digital power supply for the AD5700-1 and the field side of the isolators. Alternatively, the 5 V output low dropout (LDO) regulator on the ADuM3471 can be used. The LDO provides a tighter regulated 5 V rail; however, it does not allow for dc overvoltages of greater than 20 V due to the absolute maximum ratings on the regulator input pin of the ADuM3471.

The output connector configuration for the EVAL-CN0321-SDPZ hardware is shown in Table 1.

Table 1. Output Terminals

Terminal Name	Output Type
OUT2	Voltage output ranges
GND	Ground
OUT1	Current output ranges

HART Compatibility

The AD5700-1 is used in conjunction with the AD5422 to form a complete HART-compatible 4 mA to 20 mA solution. The AD5700-1 0.5% precision internal oscillator provides significant space savings in channel-to-channel isolated applications where a clock crystal would otherwise be needed per channel. The crystal would typically be bigger than the AD5700-1 IC itself; therefore, the internal oscillator results in significant space saving.

The HART modem output is attenuated by C1 and C2 and ac-coupled into the AD5422 via the CAP2 pin. Additional information can be found in the AN-1065 Application Note. Circuit Note CN-0278 describes an alternate HART coupling method using the $R_{\text{\tiny SET}}$ pin that offers greater power supply rejection; however, it requires an external precision current setting resistor.

Isolated Power

The voltage output headroom required by the AD5422 is $0.8\,\mathrm{V}$ maximum, and the current output needs a $2.5\,\mathrm{V}$ headroom maximum. Therefore, a >12.5 V supply is required to output a $20\,\mathrm{mA}$ current through a $500\,\Omega$ load. In this design, the minimum supply voltage (overtemperature) is no lower than $13.5\,\mathrm{V}$, which allows for some additional headroom.

The ADuM347x devices are quad-channel digital isolators with integrated pulse-width modulation (PWM) controllers and low impedance transformer drivers (X1 and X2). The only additional components required for an isolated dc-to-dc converter are a transformer and simple full-wave diode rectifier. The devices provide up to 2 W of regulated, isolated power when supplied from a 5.0 V or 3.3 V input, which eliminates the need for a separate isolated dc-to-dc converter.

The iCoupler* chip-scale transformer technology is used to isolate the logic signals, and the integrated transformer driver with isolated secondary side control provides high efficiency for the isolated dc-to-dc converter. The internal oscillator frequency is adjustable from 200 kHz to 1 MHz and is determined by the $R_{\rm OC}$ value. When $R_{\rm OC}=100~{\rm k}\Omega$, the switching frequency is 500 kHz.

The ADuM3471 regulation is from the positive 15 V supply. The feedback for regulation is from the divider network (R1 and R2). The resistors are chosen such that the feedback voltage is 1.25 V when the output voltage is 15 V. The feedback voltage is compared with the ADuM3471 internal feedback setpoint voltage of 1.25 V. Regulation is achieved by varying the duty cycle of the PWM signals driving the external transformer.

The negative supply is loosely regulated and could potentially be as low as $-26.4\,\mathrm{V}$ if unloaded. For this reason, a 25 V Zener diode was placed on the negative supply. This diode draws a small current from the supply when it is lightly loaded; however, it ensures that it clamps at around 25 V.

Another approach is to use an isolation transformer with a 4:1 turns ratio; when it is unloaded, the negative rail does not go as low. In applications that require higher compliance voltages or very low power dissipation, a different power supply design should be considered.

Input Power

The circuit in Figure 1 is powered by a $24\,\mathrm{V}$ supply. The ADP2441 is used to step the $24\,\mathrm{V}$ down to $5\,\mathrm{V}$ to supply all controller side circuitry.

The ADP2441 has a wide tolerance on its input supply, making it ideal for accepting a 24 V industrial supply. Because the ADP2441 can accept up to 36 V, reliable transient protection of the supply input is also more easily achieved.

The ADP2441 also features a number of other safety/reliability functions, such as undervoltage lockout (UVLO), a precision enable feature, a power good pin, and overcurrent limit protection. It can achieve up to 90% efficiency for an input of 24 V and an output of 5 V.

Isolation

The ADuM3471 power isolation circuitry includes four fully isolated voltage channels with a 2.5 kV isolation rating. These four channels are used to isolate the four datalines (SCLK, LATCH, SDIN, and SDO) of the AD5422. Isolation of the SDO line is not essential for the operation of the circuit; however, it does allow access to diagnostic and fault features, as well as register readback.

The ADuM3482 is a 3.75 kV quad channel digital isolator in a small 20-lead SSOP package (7.2 mm \times 7.8 mm). The ADuM3482 core operates between 3.0 V and 5.5 V, whereas the I/O supply can range from 1.8 V to 5.5 V. These devices can be used to interface directly with 1.8 V logic. This isolator is used to isolate the UART signals for the AD5700-1 HART modem.

Further information on *i*Coupler products is available at www.analog.com/icouplers.

DC Overvoltage Protection

The circuit in Figure 1 allows for continuous $+36\,\mathrm{V}$ and $-28\,\mathrm{V}$ dc overvoltage protection. This means the circuit is protected in cases where a dc power supply line is accidentally connected to the output.

During an overvoltage condition, the supplies are pulled up or down via the external protection diodes. The resistance between these diodes and the output terminals limits the peak current.

The maximum/minimum voltage on the output terminals is limited by the breakdown voltage on any circuitry connected to the output or power supplies. The current and voltage outputs of the AD5422 cantolerate +48 V downto –28 V. The AV $_{\rm SS}$ input can tolerate –28 V, and the AV $_{\rm DD}$ can tolerate +48 V. The ADR02 reference can tolerate 36 V on its supply. The ADC_IP pin of the AD5700-1 is protected by a 150 k Ω resistor that limits any current, followed by a 300 pF capacitor to block any dc current. Do not expose other ICs to higher voltages during the dc overvoltage condition.

Transient Voltage Protection

The AD5422 contains ESD protection diodes that prevent damage from normal handling. The industrial control environment can, however, subject I/O circuits to much higher transients. To protect the AD5422 from excessively high voltage transients, external power diodes and a surge current limiting resistor may be required, as is shown in Figure 1.

The constraint on the resistor value in the current output path, shown in Figure 1 as 18 Ω , is that during normal operation, the output level at $I_{\rm OUT}$ must remain within its voltage compliance limit of $AV_{\rm DD}-2.5$ V, and the two protection diodes and resistor must have the appropriate power ratings. With 18 Ω , for a 4 mA to 20 mA output, the compliance limit at the terminal is decreased by $V=I_{\rm MAX}\times R=0.36$ V.

The constraint on the resistor value in the voltage output path, shown in Figure 1 as 100 Ω , is that there must be 0.8 V headroom over the output voltage. The effect of this resistor can be minimized by using the $+V_{\text{SENSE}}$ input. Shown in Figure 1, the $+V_{\text{SENSE}}$ input is protected by a 22 Ω resistor. There is also a corresponding 22 Ω resistor on the $-V_{\text{SENSE}}$ path. These two 22 Ω resistors cause some absolute gain error that may need to be calibrated out at room temperature; the reason for this error is that there is only about 70 k Ω impedance in the internal feedback circuitry of the AD5422. The advantage of sensing the voltage at the output and not at the V_{OUT} pin of the AD5422 is that the protection resistor for the V_{OUT} pin has a varying voltage across it, depending on the load current drawn. Sensing at the terminal avoids this error source.

Further protection is provided with transient voltage suppressors (TVS) or transorbs. These are available as both unidirectional and bidirectional suppressors and in a wide range of standoff and breakdown voltage ratings. Size the TVS with the lowest breakdown voltage possible while not conducting in the functional range of the current output. As previously discussed, it is recommended that all remotely connected nodes be protected.

COMMON VARIATIONS

This circuit is proven to work well with good stability and accuracy with the component values shown. When the application needs the 4 mA to 20 mA current output only, a single-supply scheme can be used. In this case, the positive AV $_{\rm DD}$ supply for the AD 5422 can be 24 V, for example, and the output compliance is 24 V - 2.5 V = 21.5 V. With an output current of 20 mA, a load resistance as high as 1 k Ω is possible.

For applications not requiring 16-bit resolution, the 12-bit AD5412 is available. For applications that require only current outputs, the AD5420 (16-bit) and AD5410 (12-bit) are available.

For applications that require voltage and current outputs on the same terminal, see Circuit Note CN-0278 for a technique.

If overvoltage protection is not required, a reference with a lower maximum supply voltage can be used such as the ADR4550 or the ADR445.

The ADuM347x isolators (ADuM3470, ADuM3471, ADuM3472, ADuM3473, and ADuM3474) provide four independent isolation channels in a variety of input/output channel configurations. These devices are also available with either a maximum data rate of 1 Mbps (A grade) or 25 Mbps (C grade).

The AD5700 modem can be used instead of the AD5700-1; however, either an external crystal or a CMOS clock is required.

CIRCUIT EVALUATION AND TEST

Equipment Required

The following equipment is required:

- The EVAL-SDP-CB1Z system demonstration platform (SDP-B)
- The EVAL-CN0321-SDPZ evaluation board and software
- A PC (Windows® 32-bit or 64-bit)
- A 24 V power supply
- A precision voltmeter, such as Agilent 34410A
- A digital test filter (such as the HCF_TOOL-31 available from the HART Communication Foundation)
- A 500 Ω precision load resistor
- An oscilloscope, Tektronix DS1012B or equivalent

Circuit Note CN-0321

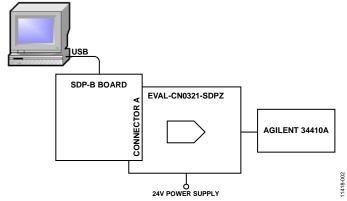


Figure 2. Test Setup Functional Diagram

Test Setup Functional Diagram

A diagram of the test setup is shown in Figure 2.

Software Installation

The evaluation kit includes self-installing software on a CD. The software is compatible with Windows XP (SP2), Vista (32-bit and 64-bit) or Windows 7 (32-bit and 64-bit). If the setup file does not run automatically, run the **setup.exe** file from the CD.

Install the evaluation software before connecting the evaluation board and SDP board to the USB port of the PC to ensure that the evaluation system is correctly recognized when connected to the PC.

- 1. Connect the EVAL-SDP-CB1Z via the USB port of the PC using the supplied cable.
- 2. Connect the EVAL-CN0321-SDPZ evaluation board to Connector A. If Connector B is used, the UART of the EVAL-SDP-CB1Z will not function as required.
- 3. Power up the EVAL-CN0321-SDPZ by applying 24 V to the J1 connector.
- 4. Start the EVAL-CN0321-SDPZ software and proceed through any dialog boxes that appear. This completes the installation.

Software

The main software window is shown in Figure 3. Click **Advanced** for more options for configuring the AD5422.

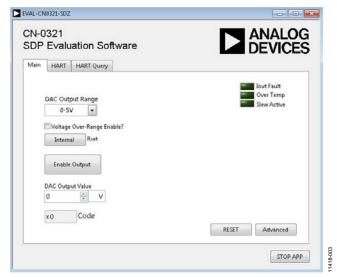


Figure 3. Main Software Window

For HART communications, ensure a current output range is enabled and then select the **HART** tab. From the **HART** tab, data can be entered into the **Command** box and sent over the 4 mA to 20 mA loop, and the software can be set to poll for any data on the 4 mA to 20 mA loop. Alternately, by selecting the **HART Query** tab, a connected HART-compatible actuator can be queried for its device address and device type.

Absolute Accuracy Performance

The specification for the total unadjusted error (TUE) for the AD5422 in current output mode using the internal R_{SET} is 0.08% FSR typical at 25°C.

The total error of the ADR02 reference (B grade) is 0.06% maximum at 25°C.

Table 2 shows the measured current output error of the circuit for the 4 mA to 20 mA range.

Table 2. Measured Current Output Error (4 m A to 20 m A Range)

Code (Hex)	Current at Output (mA)	Error (%FSR)
0000	3.992	-0.049
4000	7.995	-0.034
8000	11.997	-0.018
B000	16.000	+0.001
FFFF	20.003	+0.020

The results are well within the expected values.

Similarly, for voltage output mode, the AD 5422 TUE is 0.01% FSR typical at 25 °C.

The ADR02 reference error (B grade) is 0.06% maximum at 25°C.

Table 3 shows the measured voltage output error for the circuit in the ± 10 V output range.

Table 3. Measured Voltage Output Error (±10 V Range)

Code (Hex)	Voltage at Output (V)	Error (%FSR)
0000	-10.010	-0.050
4000	-5.005	-0.023
8000	+0.001	+0.003
B000	+5.006	+0.031
FFFF	+10.011	+0.057

The voltage output shown in Table 3 also includes the error in the circuit for the 22 Ω protection resistors on the +V_SENSE and -V_SENSE inputs of the AD 5422. The +V_SENSE and -V_SENSE inputs are internally connected to a ~70 k Ω feedback resistor. The additional 22 Ω resistors externally add a gain error of roughly 22 k $\Omega/70~k\Omega$, or 0.031%. This initial error can be removed by calibration.

Integral Nonlinearity (INL) Performance

The INL of the AD5422 was tested using both linear supplies and the isolated dc-to-dc switching supplies to ensure no loss in system accuracy was incurred because of the switching supplies. Figure 4 shows the INL for both the linear supplies and the switching supplies. There is no noticeable performance loss when using the switching supplies as compared to the linear supplies.

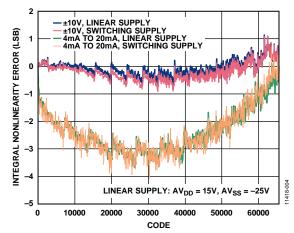


Figure 4. Measured INL of Circuit with Linear and Switching Supply

The average output noise was also tested and compared over time when using a linear supply and switching supply, as shown in Figure 5. Note that there is a slight offset in output noise measured over time. This offset is not much larger than 1 LSB and could be introduced by a slightly different measurement setup or the drift in the reference during the time between the two measurements.

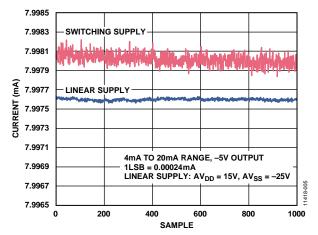


Figure 5. Measured Average DAC Output Noise, 1000 Sample, Meter Set to NPLC = 1

HART Compliance

For the circuit in Figure 1 to be HART-compliant, it must meet the HART physical layer specifications. There are a number of physical layer specifications included in the HART specification documents. For evaluating the performance of the hardware, the output noise during silence and the analog rate of change test were used.

Circuit Note CN-0321

Output Noise During Silence Test

When a HART device is not transmitting (silence), it should not couple noise onto the network. Excessive noise may interfere with the reception of HART signals by the device itself or other devices on the network.

The voltage noise measured across a 500 Ω load in the loop must contain no more than 2.2 mV rms of combined broadband and correlated noise in the HART extended frequency band. In addition, the noise must not exceed 138 mV rms outside the HART extended frequency band.

This noise was measured by a true rms meter connected across the 500 Ω load. This noise was measured directly for the out-of-band noise and measured through the HCF_TOOL-31 filter for the in-band noise. An oscilloscope was also used to examine the noise waveform.

The captured noise waveform is shown in Figure 6, and the results are summarized in Table 4.

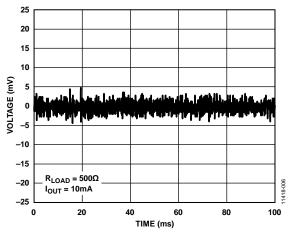


Figure 6. Output Noise During Silence Waveform

Table 4. Output Noise During Silence

Output Noise	Measured (mV)		
Outside Extended Frequency Range	0.6	<138	
Inside Extended Frequency Range	0.126	<2.2	

Analog Rate of Change

The analog rate of change test ensures that when a device regulates the analog output current, the maximum rate of change of the analog current does not interfere with HART communications. Step changes in current disrupt HART signaling.

The worst-case change in the analog output current must not produce a disturbance higher than 15 mV peak, measured across a 500 Ω load in the HART extended frequency band.

The AD5422 DAC and output driver are relatively fast. Therefore, to meet the required system specifications, the output current change is limited by the hardware slew rate limit using capacitors on the CAP1 and CAP2 pins of the AD5422 and the digital slew rate control feature of the AD5422. This is outlined in more detail in the AN-1065 Application Note.

This test was performed using an oscilloscope coupled to a 500 Ω load through the HCF_TOOL-31 filter.

The result is shown in Figure 7. The 4 mA and 20 mA output line (see blue line in Figure 7) shows the periodic steps between 4 mA and 20 mA, sensed directly across a 500 Ω load. The output of the filter \times 10 line (see red line in Figure 7) is the signal captured on the HCF_TOOL-31 filter output, amplified 10×, within the 150 mV peak limits.

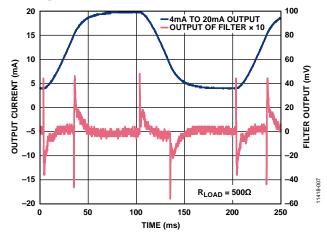


Figure 7. Analog Rate of Change Waveform

LEARN MORE

CN-0321 Design Support Package: http://www.analog.com/CN0321-DesignSupport

CN-0270, Complete 4 mA to 20 mA HART Solution

CN-0278, Complete 4 mA to 20 mA HART Solution with Additional Voltage Output Capability

Maurice Egan, Configuring the AD5420 for HART Communication Compliance, Application Note AN-1065, Analog Devices.

HART® Communication Foundation

Data Sheets and Evaluation Boards

AD5422 Data Sheet

AD5700-1 Data Sheet


ADP2441 Data Sheet

ADuM3471 Data Sheet

ADuM3482 Data Sheet

System Demonstration Platform (EVAL-SDP-CB1Z)

(Continued from first page) Circuits from the Lab circuits are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. Whileyou may use the Circuits from the Lab circuits in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab circuits. Information furnished by Analog Devices is believed to be accurate and reliable. However, Circuits from the Lab circuits are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, norfor any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any Circuits from the Lab circuits at any time without notice but is under no obligation to do so.

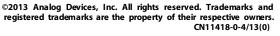





Компания «Океан Электроники» предлагает заключение долгосрочных отношений при поставках импортных электронных компонентов на взаимовыгодных условиях!

Наши преимущества:

- Поставка оригинальных импортных электронных компонентов напрямую с производств Америки, Европы и Азии, а так же с крупнейших складов мира;
- Широкая линейка поставок активных и пассивных импортных электронных компонентов (более 30 млн. наименований);
- Поставка сложных, дефицитных, либо снятых с производства позиций;
- Оперативные сроки поставки под заказ (от 5 рабочих дней);
- Экспресс доставка в любую точку России;
- Помощь Конструкторского Отдела и консультации квалифицированных инженеров;
- Техническая поддержка проекта, помощь в подборе аналогов, поставка прототипов;
- Поставка электронных компонентов под контролем ВП;
- Система менеджмента качества сертифицирована по Международному стандарту ISO 9001;
- При необходимости вся продукция военного и аэрокосмического назначения проходит испытания и сертификацию в лаборатории (по согласованию с заказчиком):
- Поставка специализированных компонентов военного и аэрокосмического уровня качества (Xilinx, Altera, Analog Devices, Intersil, Interpoint, Microsemi, Actel, Aeroflex, Peregrine, VPT, Syfer, Eurofarad, Texas Instruments, MS Kennedy, Miteq, Cobham, E2V, MA-COM, Hittite, Mini-Circuits, General Dynamics и др.);

Компания «Океан Электроники» является официальным дистрибьютором и эксклюзивным представителем в России одного из крупнейших производителей разъемов военного и аэрокосмического назначения «JONHON», а так же официальным дистрибьютором и эксклюзивным представителем в России производителя высокотехнологичных и надежных решений для передачи СВЧ сигналов «FORSTAR».



«JONHON» (основан в 1970 г.)

Разъемы специального, военного и аэрокосмического назначения:

(Применяются в военной, авиационной, аэрокосмической, морской, железнодорожной, горно- и нефтедобывающей отраслях промышленности)

«FORSTAR» (основан в 1998 г.)

ВЧ соединители, коаксиальные кабели, кабельные сборки и микроволновые компоненты:

(Применяются в телекоммуникациях гражданского и специального назначения, в средствах связи, РЛС, а так же военной, авиационной и аэрокосмической отраслях промышленности).



Телефон: 8 (812) 309-75-97 (многоканальный)

Факс: 8 (812) 320-03-32

Электронная почта: ocean@oceanchips.ru

Web: http://oceanchips.ru/

Адрес: 198099, г. Санкт-Петербург, ул. Калинина, д. 2, корп. 4, лит. А