

## MP020A-5 Offline, Primary-Side Regulator with CC/CV Control and a 700V MOSFET

The Future of Analog IC Technology

# DESCRIPTION

The MP020A-5 is an offline, primary-side regulator that provides accurate constant voltage and constant current regulation without an optocoupler or a secondary feedback circuit. The MP020A-5 has an integrated 700V MOSFET.

The MP020A-5's variable off-time control allows a flyback converter to operate in discontinuous conduction mode (DCM). The MP020A-5 also features protection functions such as VCC under-voltage lockout (UVLO), over-current protection (OCP), over-temperature protection (OTP), open-circuit protection (OCkP), and over-voltage protection (OVP). Its internal highvoltage start-up current source and powersaving technologies limit the no-load power consumption to less than 30mW.

The MP020A-5's variable switching frequency technology provides natural spectrum shaping to smooth the EMI signature, making it suitable for offline, low-power battery chargers and adapters.

The MP020A-5 is available in a SOIC8-7A package.

Dont Number	R <sub>DS(ON)</sub>	Maximum Output Power (85 - 265V <sub>AC</sub> )		
Part Number		Adapter	Open Frame	
MP020A-5GS	10Ω	5W	8W	

# FEATURES


- Primary-Side Control without Optocoupler or Secondary Feedback Circuit
- Precise Constant Current and Constant Voltage Control (CC/CV)
- Integrated 700V MOSFET with Minimal External Components
- Variable Off Time, Peak-Current Control
- 550µA High-Voltage Current Source
- 30mW No-Load Power Consumption
- Programmable Cable Compensation
- OVP, OCP, OCkP, OTP, and VCC UVLO
- Natural Spectrum Shaping for Improved EMI Signature
- Low Cost and Simple External Circuit
- Available in a SOIC8-7A Package

## APPLICATIONS

- Cell Phone Chargers
- Adapters for Handheld Electronics
- Standby and Auxiliary Power Supplies
- Small Appliances

All MPS parts are lead-free, halogen-free, and adhere to the RoHS directive. For MPS green status, please visit the MPS website under Quality Assurance. "MPS" and "The Future of Analog IC Technology" are registered trademarks of Monolithic Power Systems, Inc.

# TYPICAL APPLICATION

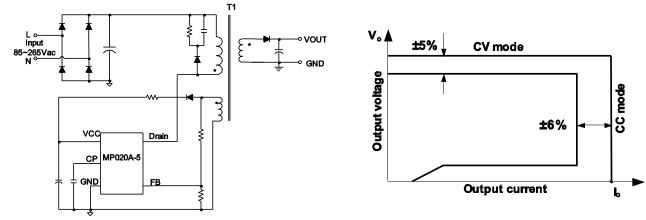

MP020A-5 Rev. 1.0 6/23/2017 MF www.MonolithicPower.com

MPS Proprietary Information. Patent Protected. Unauthorized Photocopy and Duplication Prohibited. © 2017 MPS. All Rights Reserved.



### **ORDERING INFORMATION**

Part Number*	Package	Top Marking
MP020A-5GS	SOIC8-7A	See Below


\* For Tape & Reel, add suffix -Z (e.g. MP020A-5GS-Z)

### **TOP MARKING**

MP020A-5
LLLLLLLL
MPSYWW

MP020A-5: Product code of MP020A-5GS LLLLLLL: Lot number MPS: MPS prefix Y: Year code WW: Week code

### **PACKAGE REFERENCE**

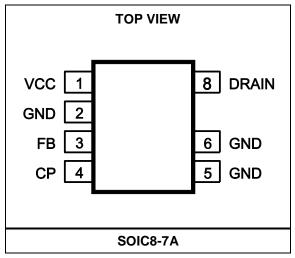

### ABSOLUTE MAXIMUM RATINGS (1)

DRAIN to GND
Continuous power dissipation $(T_A = +25^{\circ}C)$ <sup>(2)</sup> SOIC8-7A

### Recommended Operating Conditions <sup>(3)</sup>

Operating	junction temp.	(T <sub>J</sub> )40°	C to +	-125°C
Operating	VCC range		6.6V	to 28V

# Thermal Resistance $^{(4)}$ $\theta_{JA}$ $\theta_{JC}$

#### NOTES:


- 1) Exceeding these ratings may damage the device.
- 2) The maximum allowable power dissipation is a function of the maximum junction temperature T<sub>J</sub> (MAX), the junction-toambient thermal resistance  $\theta_{JA}$ , and the ambient temperature T<sub>A</sub>. The maximum allowable continuous power dissipation at any ambient temperature is calculated by P<sub>D</sub> (MAX) = (T<sub>J</sub> (MAX)-T<sub>A</sub>)/ $\theta_{JA}$ . Exceeding the maximum allowable power dissipation produces an excessive die temperature, causing the regulator to go into thermal shutdown. Internal thermal shutdown circuitry protects the device from permanent damage.
- The device is not guaranteed to function outside of its operating conditions.
- 4) Measured on JESD51-7, 4-layer PCB.

# **ELECTRICAL CHARACTERISTICS**

VCC = 15V,  $T_A = 25^{\circ}$ C, unless otherwise noted.


Parameter	Symbol	Condition	Min	Тур	Мах	Units
Supply Voltage Management	Supply Voltage Management (VCC)					
VCC on threshold	Vссн		16.8	17.3	17.8	V
VCC off threshold	VCCL		6	6.3	6.6	V
VCC operating voltage			6.6		28	V
Quiescent current	lq	At no load condition, VCC = 20V		360	410	μA
Operating current	IOP	60kHz, VCC = 20V		500		μA
Leakage current from VCC	I <sub>Leak_VCC</sub>	VCC = 0 $\rightarrow$ 16V, DRAIN floating		0.1	1	μA
Internal MOSFET (DRAIN)						
Break-down voltage	VBRDSS	$VCC = 20V, V_{FB} = 7V$	700			V
Supply current from DRAIN	ICharge	$VCC = 4V, V_{DRAIN} = 100V$	450	550	750	μA
Leakage current from DRAIN	Leak_Drain	V <sub>DS</sub> = 500V <sub>DC</sub>		1	10	μA
On-state resistance	R <sub>ON</sub>	$I_D = 10mA, T_J = 20^{\circ}C$		10	13	Ω
Minimum switching frequency	fмın	At no load condition		120		Hz
Internal Current Sense						
Current limit	Limit	V <sub>FB</sub> = -0.5V	365	380	395	mA
Leading-edge blanking	t <sub>LEB</sub>		230	300	370	ns
Feedback Input (FB)						
FB input current	I <sub>FB</sub>	$V_{FB} = 4V, V_{CP} = 3V$	10	14	18	μA
FB threshold	V <sub>FB</sub>		3.93	4	4.07	V
DCM detect threshold	V <sub>DCM</sub>		80	120	160	mV
FB open-circuit threshold	VFBOPEN		-0.22	-0.15	-0.08	V
FB OVP threshold	VFBOVP		6.2	6.35	6.5	V
OVP sample delay	tovp			3.5		μs
Output Cable Compensation	(CP)					
Cable compensation voltage	VCP	Full load		2		V
Thermal Shutdown						
Thermal shutdown threshold				150		°C
Thermal shutdown recovery threshold				120		°C

### **TYPICAL CHARACTERISTICS**

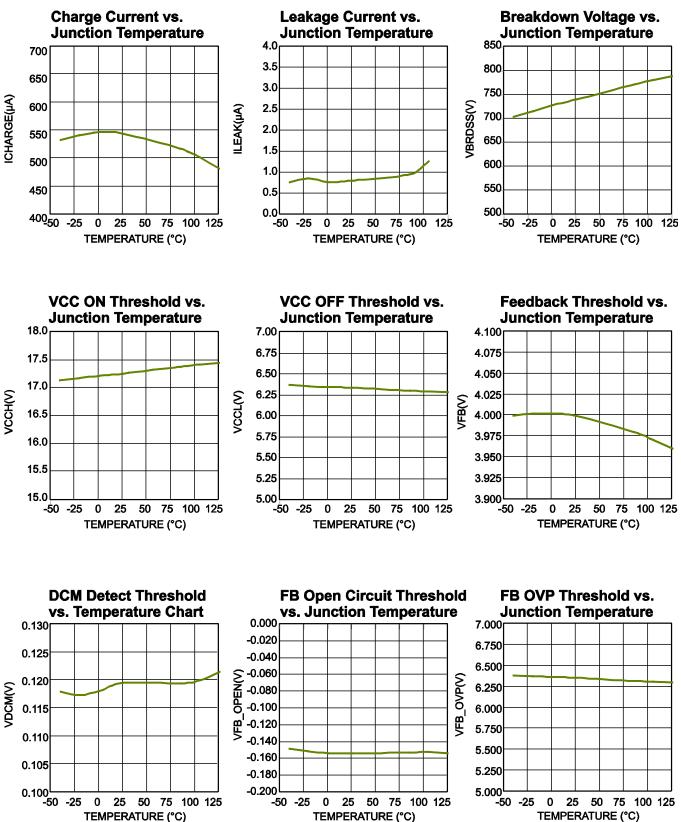


www.MonolithicPower.com MPS Proprietary Information. Patent Protected. Unauthorized Photocopy and Duplication Prohibited. © 2017 MPS. All Rights Reserved.
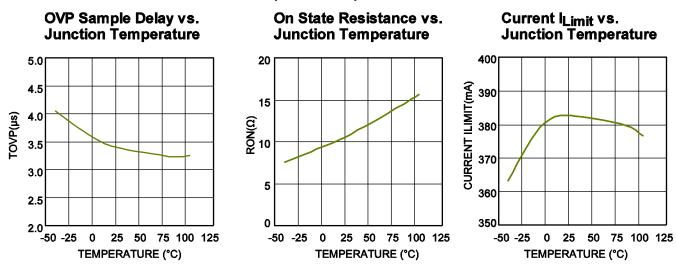
### **TYPICAL CHARACTERISTICS** (continued)


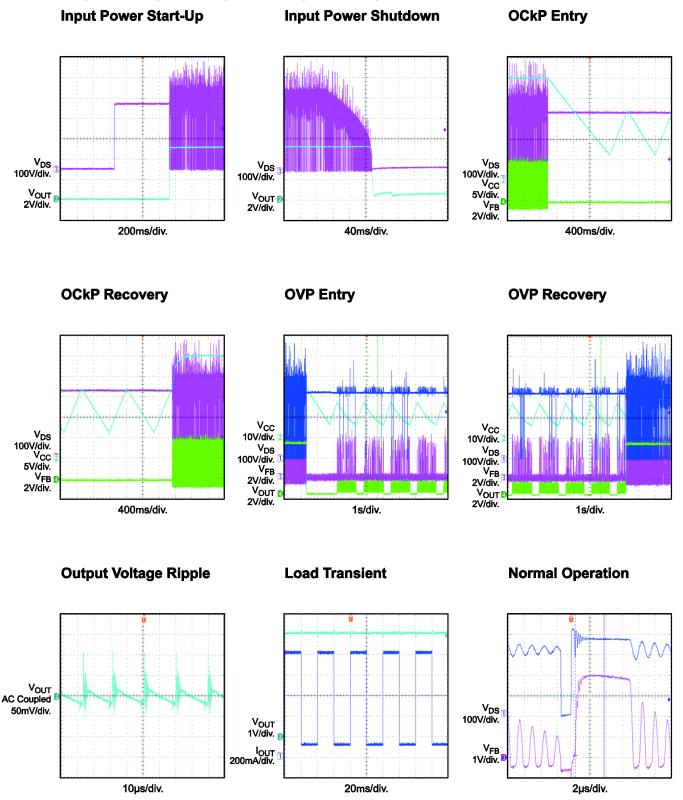
### **TYPICAL PERFORMANCE CHARACTERISTICS**


Performance waveforms are tested on the evaluation board in the Design Example section.  $V_{IN} = 230V_{AC}$ ,  $V_{OUT} = 5V$ ,  $I_{OUT} = 1A$ , L = 1.6mH,  $T_A = 25^{\circ}C$ , unless otherwise noted.



www.MonolithicPower.com MPS Proprietary Information. Patent Protected. Unauthorized Photocopy and Duplication Prohibited. © 2017 MPS. All Rights Reserved.

### **TYPICAL PERFORMANCE CHARACTERISTICS** (continued)

Performance waveforms are tested on the evaluation board in the Design Example section.  $V_{IN} = 230V_{AC}$ ,  $V_{OUT} = 5V$ ,  $I_{OUT} = 1A$ , L = 1.6mH,  $T_A = 25^{\circ}C$ , unless otherwise noted.

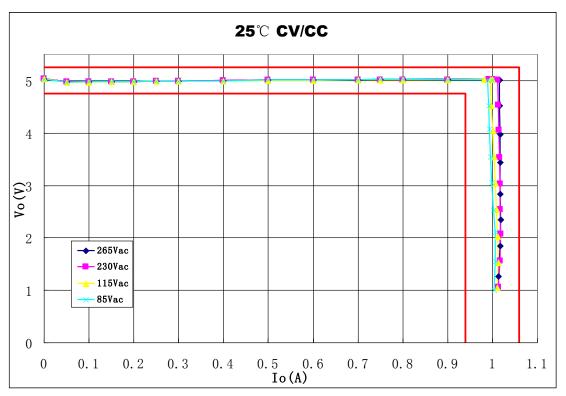

MP020A-5 CV/CC Characteristics

# **PIN FUNCTIONS**

SOIC8-7A Pin #	Name	Description	
1	VCC	<b>Supply.</b> The IC begins functioning when VCC charges to the on threshold (V <sub>CCH</sub> ) through an internal high-voltage current source. When VCC falls below the off threshold (V <sub>CCL</sub> ), the internal high-voltage current source turns on to charge VCC. Connect a $0.1\mu$ F decoupling ceramic capacitor for most applications.	
2, 5, 6	GND	Ground.	
3	FB	<b>Feedback.</b> FB provides the output reference voltage and detects the falling voltage edges to determine the operation mode (CV mode or CC mode).	
4	СР	Output cable compensation. Connect a 1µF ceramic capacitor as a low pass filter. The upper resistor of the resistor divider connected to FB adjusts the compensation voltage.	
8	DRAIN	Internal MOSFET drain. DRAIN is the input for the high-voltage start-up current source.	

# **BLOCK DIAGRAM**

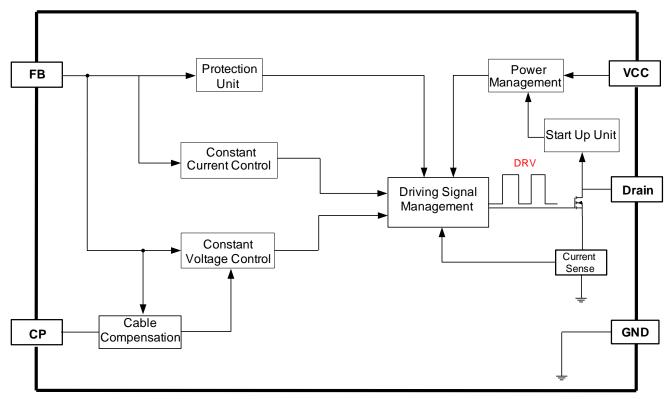


Figure 1: Functional Block Diagram

### **OPERATION**

#### Start-Up

Initially, the IC is self-supplying through an internal high-voltage current source, which is drawn from DRAIN. The internal high-voltage current source turns off for better efficiency when VCC reaches its on threshold ( $V_{CCH}$ ). Then the transformer's auxiliary winding takes over as the power source. When VCC falls below its off threshold ( $V_{CCL}$ ), the IC stops switching, and the internal high-voltage current source turns on again (see Figure ).

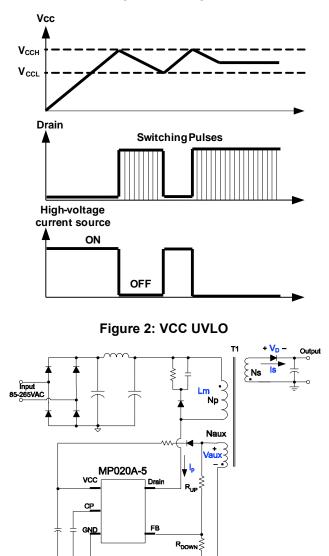


Figure 3: Simplified Flyback Converter

#### **Working Principle**

After start-up, the internal MOSFET turns on, and the current sense resistor ( $R_{CS}$ ) senses the primary current ( $i_P(t)$ ) internally (see Figure 3). The current rises linearly at a rate that can be calculated with Equation (1):

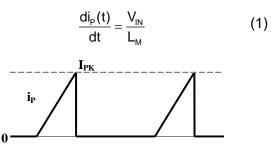


Figure 1: Primary Current Waveform

When  $i_P(t)$  rises up to  $I_{PK}$ , the internal MOSFET turns off (see Figure 4). Then the energy stored in the inductor transfers to the secondary side through the transformer.

The inductor  $(L_M)$  stores energy with each cycle as a function shown in Equation (2):

$$\mathsf{E} = \frac{1}{2} \mathsf{L}_{\mathsf{M}} \times \mathsf{I}_{\mathsf{PK}}^2 \tag{2}$$

The power transferred from the input to the output can be determined with Equation (3):

$$P = \frac{1}{2}L_{M} \times I_{PK}^{2} \times f_{S}$$
 (3)

Where  $f_{\text{S}}$  is the switching frequency. When  $I_{\text{PK}}$  is constant, the output power depends on  $f_{\text{S}.}$ 

#### **Constant Voltage (CV) Operation**

The MP020A-5 detects the auxiliary winding voltage from FB and operates in constant voltage (CV) mode to regulate the output voltage. Assume the secondary winding is the master and the auxiliary winding is the slave. When the secondary-side diode turns on, the FB voltage can be calculated with Equation (4):

$$V_{FB} = \frac{N_{P_AU}}{N_S} \times (V_O + V_D) \times \frac{R_{DOWN}}{R_{UP} + R_{DOWN}}$$
(4)

Where  $V_D$  is the secondary-side diode forwarddrop voltage, Vo is the output voltage,  $N_{P_AU}$  is the number of auxiliary winding turns,  $N_S$  is the number of secondary side winding turns, and  $R_{UP}$  and  $R_{DOWN}$  are the resistor divider for sampling.

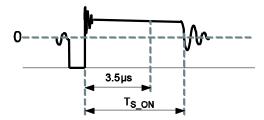


Figure 2: Auxiliary Voltage Waveform

The output voltage differs from the secondary voltage due to the current-dependent forwarddiode voltage drop. If the secondary voltage is always detected at a fixed secondary current, the difference between the output voltage and the secondary voltage is a fixed  $V_D$ . The MP020A-5 samples the auxiliary winding voltage 3.5µs after the primary switch turns off (see Figure 5). The CV loop control function turns the secondary-side diode off to regulate the output voltage.

#### **Constant Current (CC) Operation**

Figure 3 shows the constant-current operation.

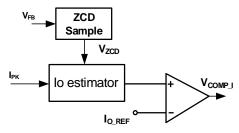


Figure 3: CC Control Loop

The flyback always works in discontinuous conduction mode (DCM), and the zero-current detection (ZCD) sample block can detect the duty cycle of the secondary-side diode.

In constant current (CC) operation, the product of  $V_{ZCD}$  times  $I_{pk}$  approximately equals  $I_{O_REF}$ , as shown in Equation (5):

$$I_{O_{REF}} = V_{ZCD} \times I_{PK}$$
 (5)

The calculated output current from the  $I_{O}$  estimator block is compared with the reference value ( $I_{O,REF}$ ), and the error signal ( $V_{COMP_I}$ ) controls the turn-on signal of the integral MOSFET.  $I_{O}$  can be calculated with Equation (6):

$$I_{O} = \frac{1}{2} \times \frac{N_{P}}{N_{S}} \times I_{O_{-REF}}$$
(6)

The MP020A-5 maintains I<sub>O\_REF</sub> at 0.152A.

### Leading-Edge Blanking

The parasitic capacitances induce a spike on the sense resistor when the power switch turns on. The MP020A-5 includes a 300ns leadingedge blanking period to avoid falsely terminating the switching pulse. During this blanking period, the current sense comparator is disabled, and the gate driver cannot switch off (see Figure 4).

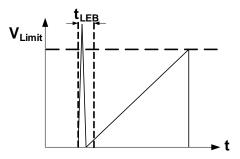


Figure 4: Leading-Edge Blanking

#### **DCM Detection**

The MP020A-5 operates in DCM in both CV and CC modes. To avoid operating in continuous conduction mode (CCM), the MP020A-5 detects the falling edge of the FB input voltage with each cycle. If the chip does not detect a 120mV falling edge, it stops switching.

#### OVP and OCkP

The MP020A-5 includes over-voltage protection (OVP) and open-circuit protection (OCkP). If the voltage at FB exceeds 6.35V for 3.5µs, or the FB input's 0.15V falling edge cannot be monitored, the MP020A-5 immediately shuts off the driving signals and enters hiccup mode. The MP020A-5 resumes normal operation when the fault has been removed.

#### **Thermal Shutdown**

When the temperature of the IC exceeds 150°C, over-temperature protection (OTP) is triggered, and the IC enters auto-recovery mode. When the temperature falls below 120°C, the IC recovers.

#### **Output Cable Compensation**

To compensate for the secondary-side cable voltage drop for a more precise output voltage, the MP020A-5 has an internal output cable compensation circuit (see Figure 5). The internal ZCD sample can detect the duty of the secondary-side diode. A low-pass filter converts the duty signal to a DC voltage ( $V_{CP}$ ) that changes as the load current varies.

 $V_{CP}$  can be converted to a current signal drawn from FB. The voltage drop on  $R_{UP}$  helps the output cable compensation. When the system operates in the maximum load, the CP voltage reaches a maximum of 2V.

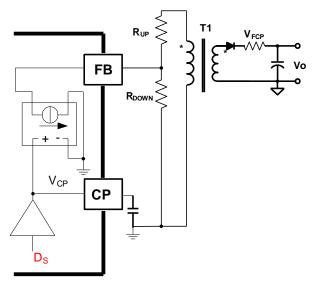


Figure 5: Output Cable Compensator

Determine the compensation voltage with Equation (7):


$$V_{\text{FCP}} = \frac{5.6 \times D_{\text{S}}}{360 \times 10^{3}} \times 2 \times R_{\text{UP}} \times \frac{N_{\text{S}}}{N_{\text{P}_{\text{AU}}}}$$
(7)

Where VFCP is the secondary-side compensation voltage drop, D<sub>s</sub> is the secondary-diode duty cycle in CC mode (0.4 for the MP020A-5), R<sub>UP</sub> is the upper resistor of the resistor divider. Ns is the number of turns for the secondary-side transformer windings, and NP AU is the number of transformer auxiliary winding turns.

### **APPLICATION INFORMATION**

#### Input Filter

The input filter helps convert the AC input to a DC source through the rectifier. Figure 6 shows the input filter, and Figure 7 shows the typical DC bus voltage waveform.

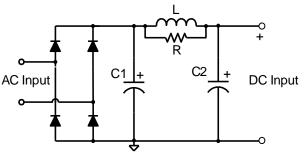

**Figure 6: Input Filter** 

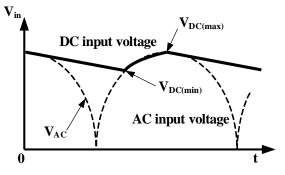


Figure 7: DC Input Voltage Waveform

Bulk capacitors (C1 and C2) filter the rectified AC input. The inductor (L) forms a  $\pi$  filter with C1 and C2 to restrain the differential mode EMI noise. The resistor (R) parallel with L restrains the mid-frequency band EMI noise. Normally, R is 1 - 10kΩ.

C1 and C2 are usually set as 2µF/W to 3µF/W for the universal input condition. For  $230V_{AC}$ single-range applications, halve the capacitor values. Avoid using very low minimum DC voltages to ensure that the converter can supply the maximum power load, which can be calculated with Equation (8):

$$V_{DC(min)} \ge \frac{N_{P}}{N_{S}} \cdot (V_{O} + V_{D}) \cdot \frac{D_{S}}{1 - D_{S}}$$
(8)

If V<sub>DC(min)</sub> cannot satisfy this expression, increase the value of the input capacitors to increase V<sub>DC(min)</sub>.

#### **Output Capacitor**

Use low ESR or very low ESR output capacitors to meet the output voltage ripple requirement without using an LC post filter. Using low ESR capacitors improves output voltage regulation and feedback voltage sampling at high temperatures or low temperatures. Use an output capacitor with an ESR below 100mΩ for better efficiency over high ESR output capacitors.

#### **Output Diode**

Use a Schottky diode because of its fast switching speed and low forward-voltage drop for better high- or low-temperature CV regulation and efficiency.

If the lower average efficiency (3% to 4%) is sufficient, replace the output diode with a fast or ultra-fast diode to reduce costs. Be sure to readjust the resistor divider values to the correct output voltage because the forward voltage drop is higher than the Schottky diode's.

#### Leakage Inductance

The transformer's leakage inductance decreases the system efficiency and affects the output current or voltage constant precision. Optimize the transformer structure to minimize the leakage inductance. Aim for a leakage inductance less than 5% of the primary inductance.

#### **RCD Snubber**

The transformer's leakage inductance causes the MOSFET drain voltage to spike and excessive ringing on the drain voltage waveform, which affects the output voltage sampling 3.5µs after the MOSFET turns off.

The RCD snubber circuit can limit the DRAIN voltage spike. Figure 8 shows the RCD snubber circuit.

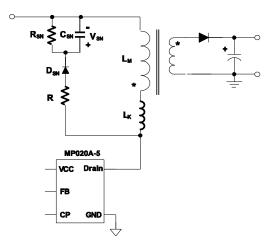


Figure 8: RCD Snubber

Select  $R_{SN}$  and  $C_{SN}$  to meet the voltage spike requirements and improve system operation.

The power dissipated in the snubber circuit can be approximated with Equation (9):

$$P_{SN} = \frac{1}{2} \cdot L_{K} \cdot I_{PK}^{2} \cdot \frac{V_{SN}}{V_{SN} - N_{PS} \times V_{O}} \times f_{S}$$
(9)

Where  $L_K$  is the leakage inductance,  $V_{SN}$  is the clamp voltage, and  $N_{PS}$  is the turn ratio of primary and secondary side.

Since  $R_{SN}$  consumes the majority of the power,  $R_{SN}$  is approximated with Equation (10):

$$R_{SN} = \frac{V_{SN}^{2}}{P_{SN}}$$
(10)

The maximum ripple of the snubber capacitor voltage can then be calculated with Equation (11):

$$\Delta V_{\rm SN} = \frac{V_{\rm SN}}{C_{\rm SN} \cdot R_{\rm SN} \cdot f_{\rm S}}$$
(11)

Generally, a 15% ripple is reasonable, so  $C_{SN}$  can be estimated with Equation (11) as well.

Normally, select a time constant ( $\tau = R_{SN} \times C_{SN}$ ) below 0.1ms for better CV sampling. Adjust the resistor based on the power loss and the acceptable clamp voltage in practical applications. The damping resistor in series with the RCD has a relatively large value to prevent any excessive voltage ringing that can affect the CV sampling and increase the output ripple. Use a 200 -  $500\Omega$  damping resistor to restrain the drain-voltage ringing.

#### **Divided Resistor**

For better application performance, select the resistor divider's total value to be between 40 -  $100k\Omega$ . Smaller resistors draw larger currents from the auxiliary winding, which increases the no-load consumption. Larger resistors may also pick up noise from adjacent components.

If necessary, use a resistor between  $1k\Omega$  and  $2k\Omega$  connected between the FB and resistor divider. R<sub>FB</sub> can also limit substrate injection current effects (see Figure 9).

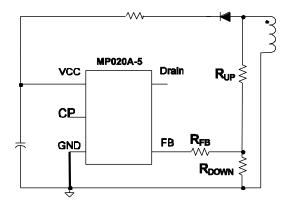


Figure 9: Feedback Resistor Divider Circuit

For more accurate CV regulation, the accuracy of these feedback resistors should be at least 1%.

#### **Dummy Load**

When the system operates without a load and no dummy load, the output voltage rises above the normal operation because of the minimum switching frequency limitation. Use a dummy load for good load regulation. However, a large dummy load deteriorates efficiency and no-load consumption, so selecting the dummy load is tradeoff between efficiency and load regulation. For most applications, use a dummy load around 10mW, which satisfies the 30mW requirement.

#### **Maximum Switching Frequency**

Use a secondary-side diode conduction time that exceeds  $5.4\mu s$ , as shown in Equation (12):


$$T_{S_{ON}} = I_{PK} \cdot \frac{N_{S} \cdot L_{M}}{N_{P} \cdot (V_{O} + V_{D})} > 5.4 \mu s$$
 (12)

For high- or low-temperature applications, select a maximum switching frequency below 75kHz.


#### **PCB Layout Guide**

Efficient PCB layout is critical for reliable operation, good EMI, and good thermal performance. For best results, refer to Figure 10 and follow the guidelines below.

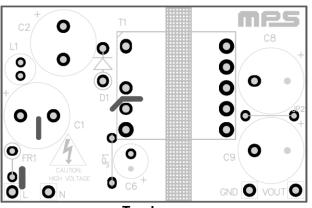- 1. Minimize the loop area formed by the input capacitor, the MP020A-5 drain-source, and the primary winding to reduce EMI noise.
- 2. Provide at least 1in<sup>2</sup> of top-side copper for adequate heat-sinking.
- 3. The copper area connected to GND is the heat conduction path for the MP020A-5.
- 4. Minimize the clamp circuit loop to reduce EMI.
- 5. Minimize the secondary loop area of the output diode and output filter to reduce EMI noise.
- 6. Provide sufficient copper area at the anode and cathode terminal of the output diode to act as a heat sink.
- 7. Place the AC input away from the switching nodes to minimize the noise coupling that may bypass the input filter.
- 8. Place the bypass capacitor as close as possible to the IC and source.
- 9. Place the feedback resistors next to FB.
- 10. Minimize the feedback sampling loop to minimize noise coupling.
- 11. Use a single-point connection at the negative terminal of the input filter capacitor for the MP020A-5 source pin and bias winding return.



Top Layer

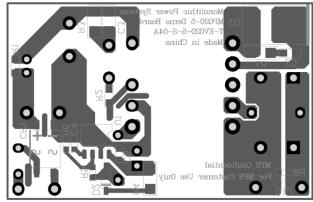

Bottom Layer Figure 10: Recommended Layout

#### **Design Example**

Table 1 shows a design example following the application guidelines based the specifications below.

····· J ···· J ····· J ······			
V <sub>IN</sub>	85 ~ 265V <sub>AC</sub>		
V <sub>OUT</sub>	5V		
I <sub>OUT</sub>	1A		
f <sub>s</sub>	60kHz		

Table 1: Design Example

Figure 14 through Figure 16 show the detailed application schematic. This circuit was used for the typical performance and circuit waveforms. For more device applications, please refer to the related evaluation board datasheets.

The transformer structure used in Figure 14 can benefit from passing the 3-wire conducted EMI test (output GND connect to earth) without the Y-cap. The Y-cap results in leakage current, which is prohibited in some cell phone charger applications. Figure 15 illustrates how the common noise of the secondary-side diode is restrained. The secondary-side winding splits to two separate windings ( $N_{SEC1}$  and  $N_{SEC2}$ ), which

www.MonolithicPower.com

MPS Proprietary Information. Patent Protected. Unauthorized Photocopy and Duplication Prohibited. © 2017 MPS. All Rights Reserved. have the same turns and approximate parasitic capacitors ( $C_{SP1}$  and  $C_{SP2}$ ), but their hot spot is opposite (Point 9 and Point 10 in Figure 15). Therefore, the common mode noise current produced at the secondary-side windings can counteract each other.

The transformer structure is simple if the application does not need to pass the 3-wire conducted EMI or uses a Y-cap. Figure 16 shows a schematic with a simple transformer structure.

# **TYPICAL APPLICATION CIRCUITS**

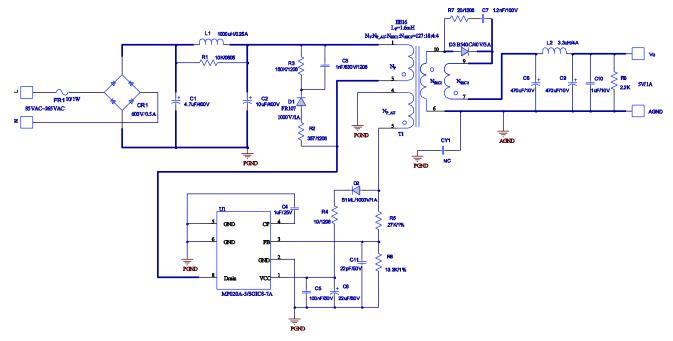


Figure 11: 5V/1A with Complicated Transformer Structure


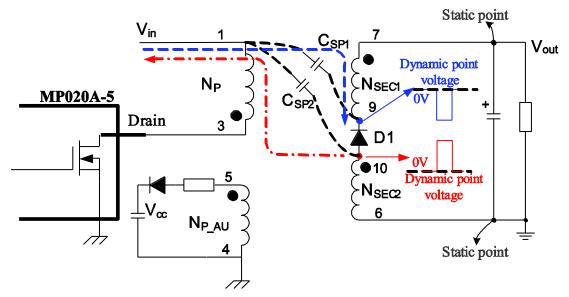


Figure 15: Secondary Side Windings Structure to Restrain the Common Mode Noise


# **TYPICAL APPLICATION CIRCUITS**

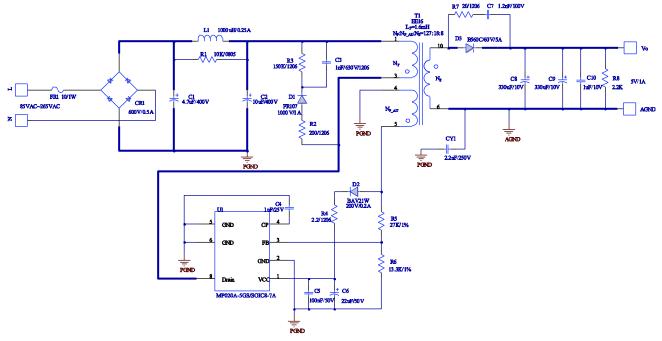






### **FLOW CHART**

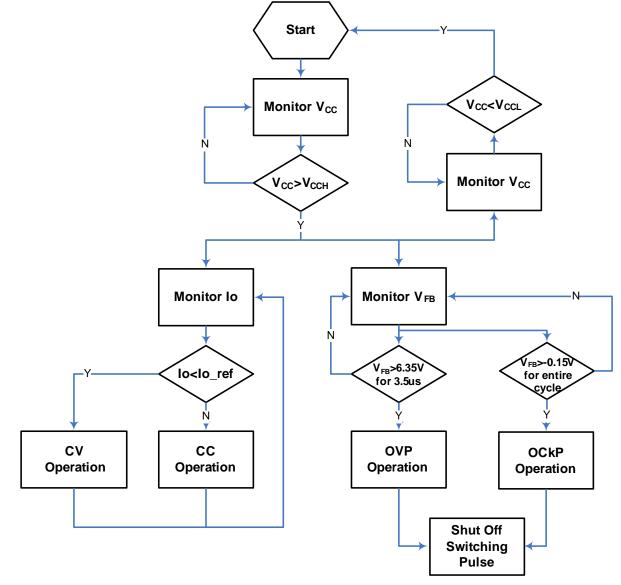



# **PACKAGE INFORMATION**

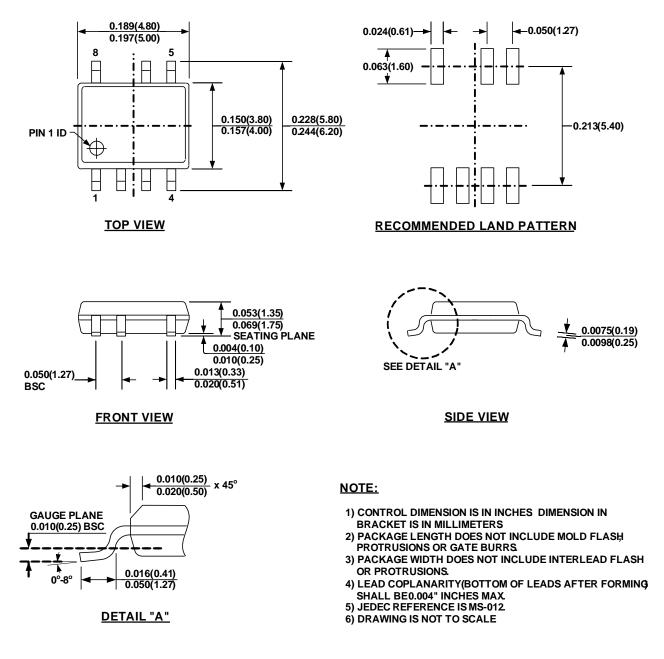

SOIC8-7A

**NOTICE:** The information in this document is subject to change without notice. Users should warrant and guarantee that third party Intellectual Property rights are not infringed upon when integrating MPS products into any application. MPS will not assume any legal responsibility for any said applications.



Компания «Океан Электроники» предлагает заключение долгосрочных отношений при поставках импортных электронных компонентов на взаимовыгодных условиях!

Наши преимущества:

- Поставка оригинальных импортных электронных компонентов напрямую с производств Америки, Европы и Азии, а так же с крупнейших складов мира;

- Широкая линейка поставок активных и пассивных импортных электронных компонентов (более 30 млн. наименований);

- Поставка сложных, дефицитных, либо снятых с производства позиций;
- Оперативные сроки поставки под заказ (от 5 рабочих дней);
- Экспресс доставка в любую точку России;
- Помощь Конструкторского Отдела и консультации квалифицированных инженеров;
- Техническая поддержка проекта, помощь в подборе аналогов, поставка прототипов;
- Поставка электронных компонентов под контролем ВП;
- Система менеджмента качества сертифицирована по Международному стандарту ISO 9001;

- При необходимости вся продукция военного и аэрокосмического назначения проходит испытания и сертификацию в лаборатории (по согласованию с заказчиком):

- Поставка специализированных компонентов военного и аэрокосмического уровня качества (Xilinx, Altera, Analog Devices, Intersil, Interpoint, Microsemi, Actel, Aeroflex, Peregrine, VPT, Syfer, Eurofarad, Texas Instruments, MS Kennedy, Miteq, Cobham, E2V, MA-COM, Hittite, Mini-Circuits, General Dynamics и др.);

Компания «Океан Электроники» является официальным дистрибьютором и эксклюзивным представителем в России одного из крупнейших производителей разъемов военного и аэрокосмического назначения «JONHON», а так же официальным дистрибьютором и эксклюзивным представителем в России производителя высокотехнологичных и надежных решений для передачи СВЧ сигналов «FORSTAR».



«JONHON» (основан в 1970 г.)

Разъемы специального, военного и аэрокосмического назначения:

(Применяются в военной, авиационной, аэрокосмической, морской, железнодорожной, горно- и нефтедобывающей отраслях промышленности)

«FORSTAR» (основан в 1998 г.)

ВЧ соединители, коаксиальные кабели, кабельные сборки и микроволновые компоненты:

(Применяются в телекоммуникациях гражданского и специального назначения, в средствах связи, РЛС, а так же военной, авиационной и аэрокосмической отраслях промышленности).



Телефон: 8 (812) 309-75-97 (многоканальный) Факс: 8 (812) 320-03-32 Электронная почта: ocean@oceanchips.ru Web: http://oceanchips.ru/ Адрес: 198099, г. Санкт-Петербург, ул. Калинина, д. 2, корп. 4, лит. А